HIGH TECH LOW LIFE \\ USB KEYBOARD TO BLUETOOTH WIRELESS CONVERSION



Not all charge circuits are created equal!

I found this out through trial and error $_{ extsf{n}}$ testing different ones to see how they performed

Some will always be on when a load is applied and you cannot turn them off[¬] This is not ideal for the 'soft power button' setup• If you use one of these boards¬ you will need a way to interrupt power to the battery (or the wireless module) to 'turn off' the keyboard to save power•

Most will not allow you to turn off the device when charging, however I did find one board that did, which could be nice for charging faster by disabling the output so all the input charge is fed to the battery without any drain (I've heard this is also better for the batteries) Although all the boards I have tested do allow 'pass through' charging meaning you can apply a load and charge at the same time. Some boards however may not, which could get annoying if you cannot use your keyboard while you are charging.



Next I wanted to figure out a way to have the option of going wired as well as wireless.

There might be some scenarios where the computer you were interfacing didn't have a BT card or there might be times where you just didn't want to use wireless at all.

I thought it would be easy just to splice the data lines (green and white) going into the keyboard, so I would need a way to turn off the BT module by wiring a slide switch to cut power to the entire BT module. This did work as expected, however I realized that there was an issue in a scenario where you still wanted to use BT but also use the PC to charge the keyboard. I realize this is an edge-case scenario but I also wanted to see if I could figure out a solution.





I also had a big brain moment where I realized I could do away with needing two separate switch (power and turning the BT module off) by hijacking the onboard LED flashlight toggle to be the switch that turns the BT module on and off, then all you would need for full functionality is just the small single pushbutton switch.

This was initially a success because it worked as expected on the first board I made₁ but the second board I made using this method was turning the BT module on and off randomly. This would cause the computer to flip flop between connecting wired and wirelessly over and over in a loop.

I figured out the problem was again due to not all charge circuits being created equal[¬] even the same exact model of charge circuit PCB must have some variance in amperage output for this LED circuit as the rated output is 50 milliamps. The amerage requirements for the BT module is also 50ma¬ so I suspect that since it's right on the cusp some will fluctuate.

This may work for you but it's not reliable in my testing¬ so next I figured out a way to solve for that problem.



Workarounds are to carry two cables - one charge cable only, one data and charge If you wanted to charge from the PC while also using BT, you'd need to use the charge cable only - this gets around the flip flop glitch







// REFINEMENT //



// COMPLETION //



Running through all of these combinations I finally read the manual in-depth - always RTFM first.

I realized that the BT module already comes with a wired / wireless toggle internally via the firmware and is activated by a hotkey on the keyboard. Through my testing I have found that it somehow just 'knows' whether it's plugged in to a PC or not and changes accordingly. I suppose if you wanted the scenario where you wanted to plug it into a PC for charging but use the wireless you could toggle the switch manually via the hotkey.

There are some caveats to wiring this this way though. One is that it's not a native direct USB connection, the BT module acts as a bridge. This will be fine for most users, but if your keyboard has firmware you can update, you cannot use this method as the PID of the board will not be recognized because it's running through the bridge. Another downside is that using the bridge limits the key rollover to 6 key (6KR0) so if your keyboard does output NKR0 via USB this will limit it. A lot of keyboards will only do 6KR0 so this isn't really a limitation and most users do not need NKR0 so it's a moot point, but it's worth mentioning.

This method is the way I would recommend most people wire up their keyboardsı it's much simpler and less components are used.



I thought I was done, but it turns out that when trying the OOL schematic method did not work on a WASD V3 (CODE V3). Due to the hardware changes to get it to work you need to intersect both the white and green data lines. Previously the V2 keyboards only needed to intersect the white data line. Depending on the keyboard you're using you may be able to get away with only toggling the white data line off, but if you run into issues most likely you will need to toggle both wires.

This is the setup you want if you want all the features + native wired connection, all from the single pushbutton switch. My later revisions included leaving the flashlight LED and drilling a hole as a tiny port as another visual indicator that 'wired' mode was initiated. I also drilled two smaller holes underneath the BT module for visual indication of BT operation, plus more LEDs and blinking lights looks cooler.